

Project Goals

- Give you a chance to exercise your skills by laying out a board
- Provide something useful for this class and other projects

This is *not* a circuit design exercise, or a detailed Arduino tutorial.

I'll give a very quick intro to Arduinos, microcontrollers, and analog/digital conversion to orient you.

The meat of the project is your work designing a simple PCB given a sketched schematic.

You will turn in:

- KiCAD project with complete schematic (required)
- KiCAD PCB layout (extra credit).

Problem Description, Specifications

Problem: The Arduino Uno (TM) is very convenient, but the analog input and output functions have (very) poor performance.

Specifications for new Shield board:



- 4 analog input and 4 analog output channels
- Improved resolution
- Improved sampling rate
- Improved S/N (signal-to-noise ratio)

This design can easily be enhanced with active filters, etc.

Quick Introduction



To ADCs, DACs, Arduinos, etc

Digital to Analog converter (DAC)

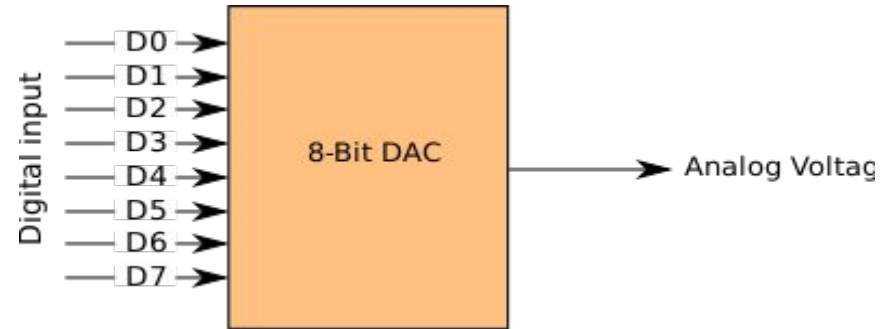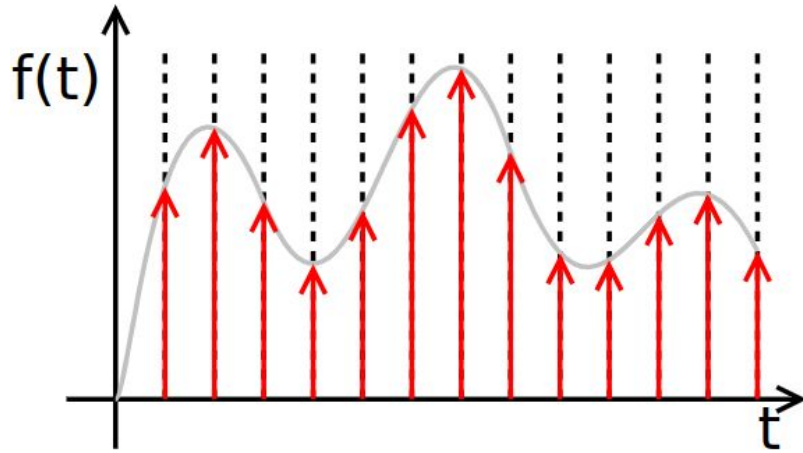

(Wikipedia: "A DAC converts an abstract finite-precision number (usually a fixed-point binary number) into a physical quantity.) In instrumentation, the output of a DAC is almost always a voltage or current.


Analog(ue) to Digital converter (ADC)

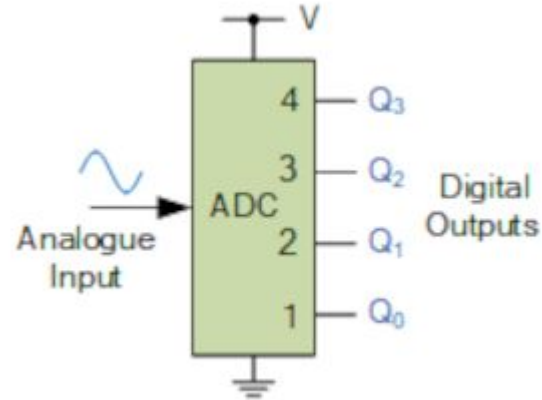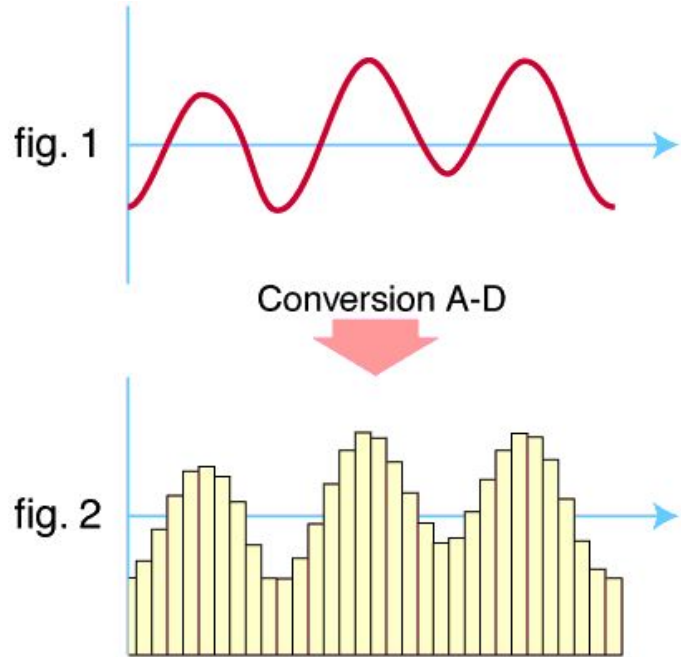

(Wikipedia: In electronics, an analog-to-digital converter (ADC, A/D, or A-to-D) is a system that converts an analog signal, such as a sound picked up by a microphone or light entering a digital camera, into a digital signal.)

Arduino Uno

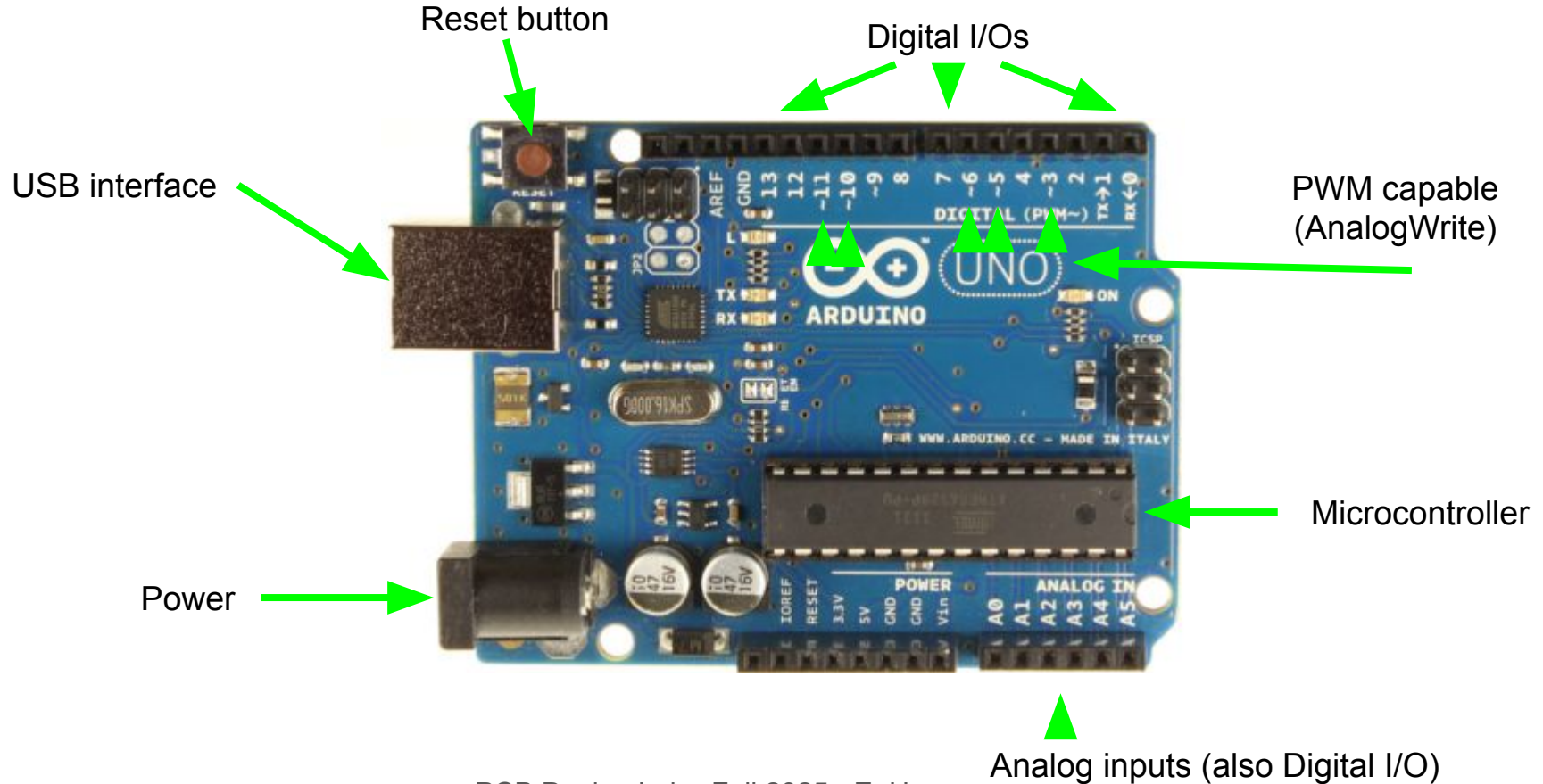Note that many types have special-functions on some pins



Arduino “shield” board

- Mounts on top of Arduino
- Uses power (usually) from Arduino
- connected using tall header pins

Multiple shields can be stacked (if they are compatible).

This is not a very sophisticated system but it does work for simple things and is a quick way to add electronics to a microcontroller.



What you're going to design

Details details:

- 4 channels analog output, 12 bits, 0-5V range
 - Buffered voltage outputs
 - Up to 75kHz update rate (software/arduino dependent)
- 4 channels analog input, 12 bits, 0-5V range
 - High-impedance voltage input
 - Up to 100kHz sampling rate (software/arduino dependent)
- Screw terminal and header connectors

SPI (Serial Peripheral Interface)

SPI is a *de facto* standard for synchronous serial communication between integrated circuits.

Typically used to communicate between microcontrollers (e.g. Arduino) and peripheral devices (DACs, ADCs, displays, EEPROM etc).



The signal and device naming is in flux and somewhat confusing. I prefer the names in bold.

There is one **Master** (Main, **Controller...**) device and one or more **Slave** (Sub, **Peripheral...**) devices

SCLK / SCK Serial clock from Main/Controller

MOSI / **COPI** Serial data from Main to Sub
Main Out Sub In
Controller Out Peripheral In

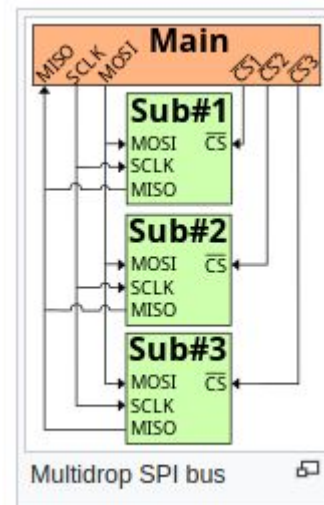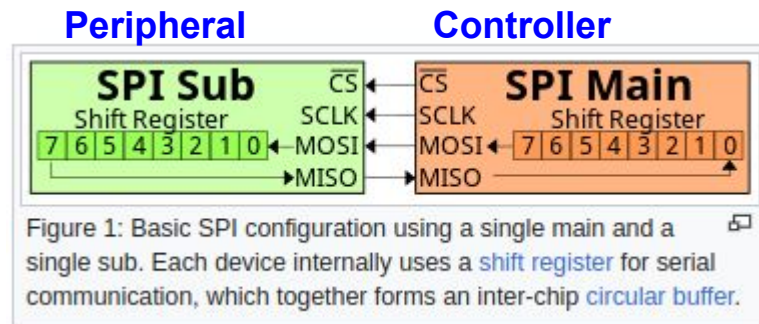MISO / **CIFO** Serial data from Sub to Main
Main In Sub Out
Controller In Peripheral Out




Arduino connections:


- Connect all GND to shield
- Use dedicated pins for SPI
- Use +5V to power external devices (low current)

+5V Pin
(limited current)

GND
Pins

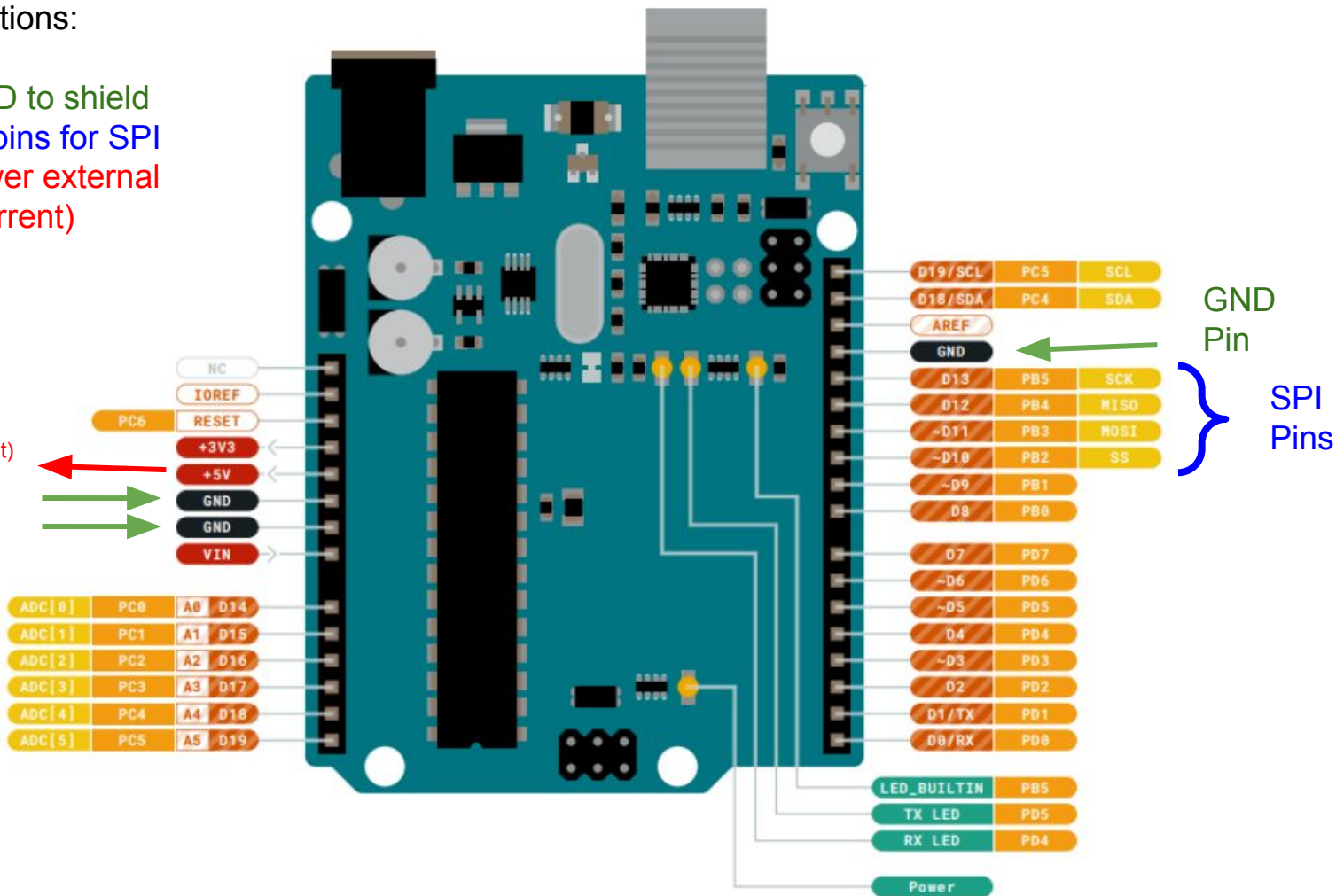


Analog In

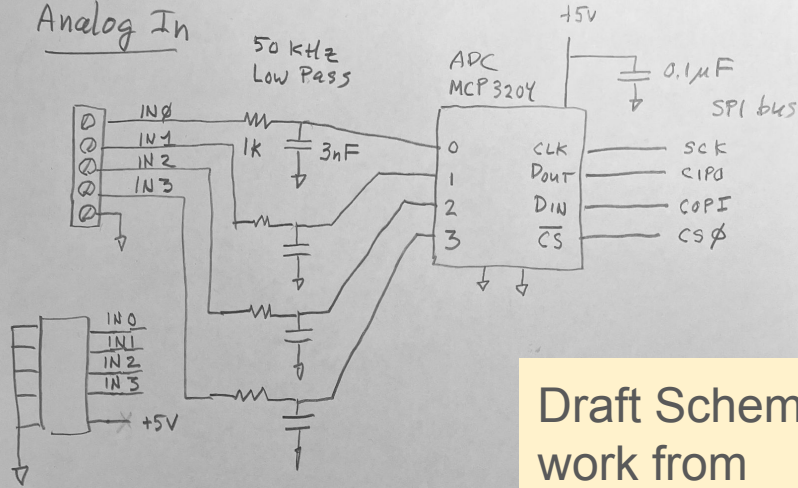


Draft Schematic for you to work from

Analog Out

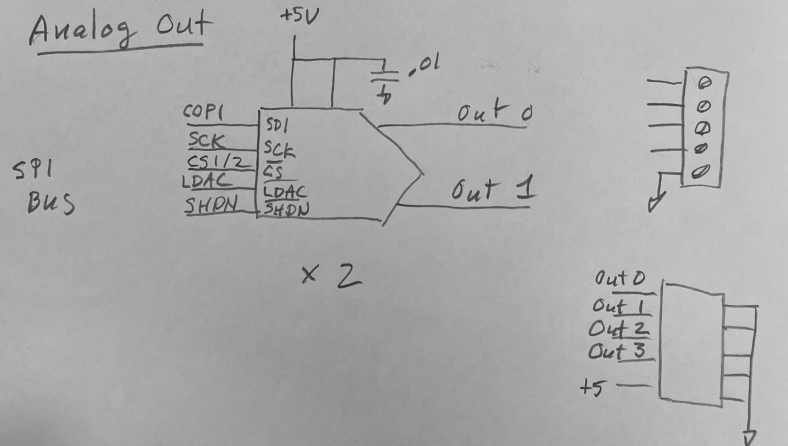

Arduino

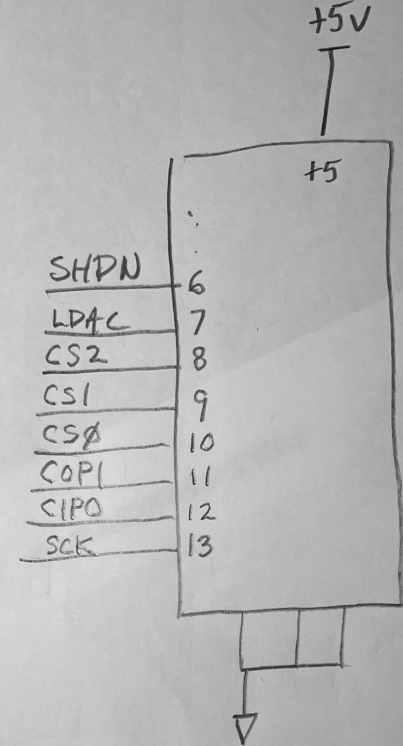

Parts

Screw terminal DigiKey ED10564-ND



A/D Converter DigiKey MCP3204-CI/P-ND



D/A Converter DigiKey MCP4922-E/P-ND



Header DigiKey 1849-FR20205VBDN-ND



I recommend the websites
of DigiKey and Mouser
for electronic parts and data

Oscilloscope-Clock/Clock.ino a x OSTVN05A150 On Shore Tech x PCB Design Lab Project - Ardu x PCB D

← → ↺ ↻ ↵ digikey.com/en/products/detail/on-shore-technology-inc/OSTVN05A150/15888... ☆

H B M WX 4 Cal Maps FPGAs Miata Work Prog MDwiki Eric's

DigiKey

All Products ▾ ED10564-ND 🔍

Products ▾ Manufacturers ▾ Resources ▾

Product Index > Connectors, Interconnects > Terminal Blocks > Wire to Board > On Shore Technology Inc. OSTVN05A150

OSTVN05A150

Digi-Key Part Number ED10564-ND

Manufacturer On Shore Technology Inc.

Manufacturer Product Number OSTVN05A150

Description TERM BLK 5P SIDE ENT 2.54MM PCB

Manufacturer Standard Lead Time 8 Weeks

Detailed Description 5 Position Wire to Board Terminal Block Horizontal with Board 0.100" (2.54mm) Through Hole

Customer Reference


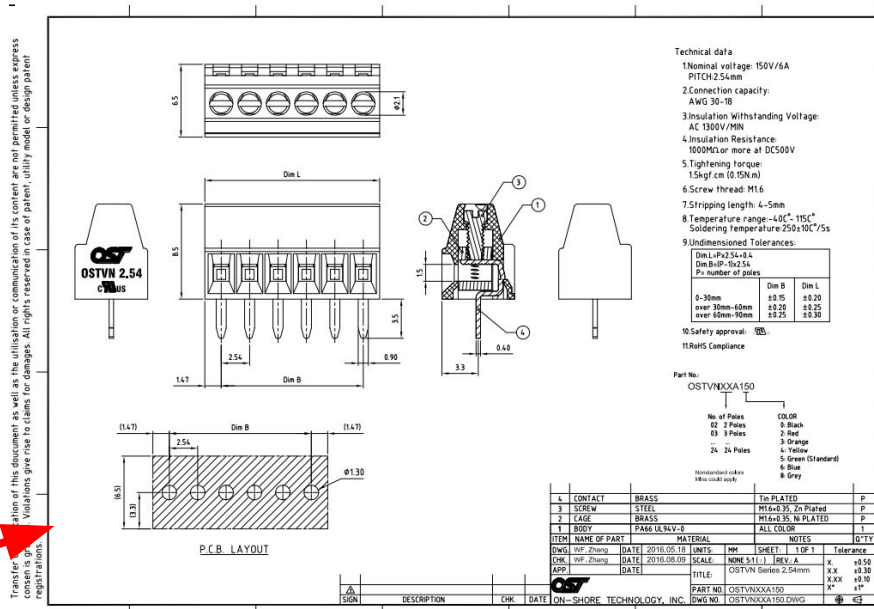
Datasheet  [Datasheet](#)

Image shown is a representation only. Exact specifications should be obtained from the product data sheet.


360°

360°




Here is my schematic.

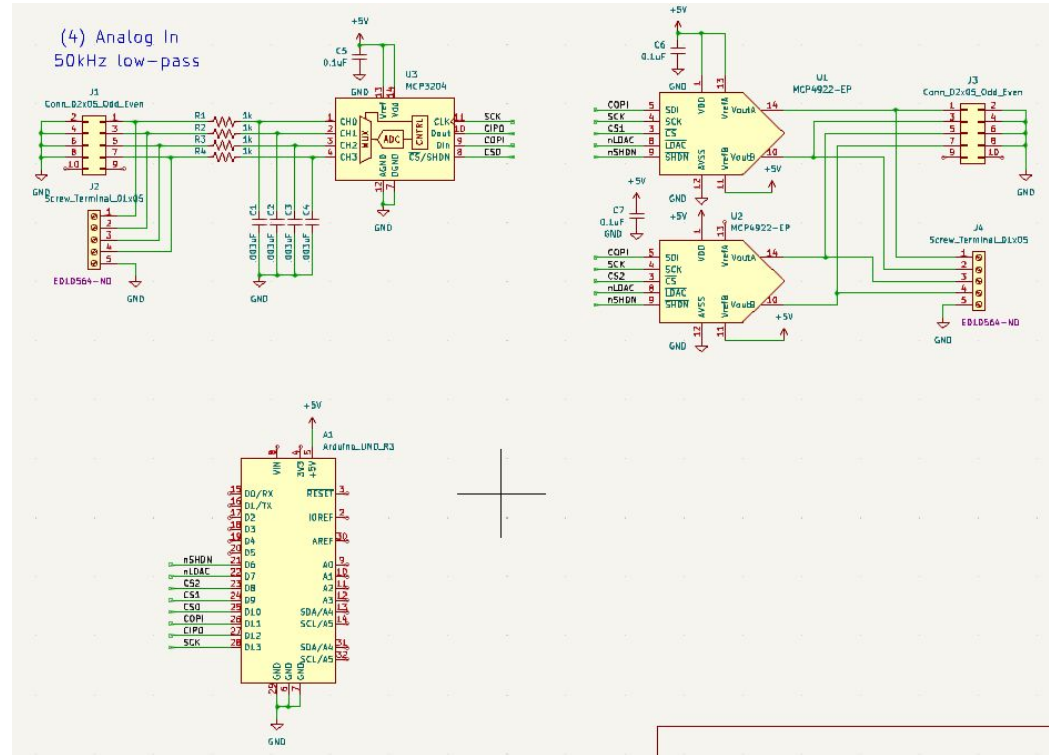It's small and fuzz on purpose :)
please don't try to copy it exactly
but make your own.



Here is the finished product...

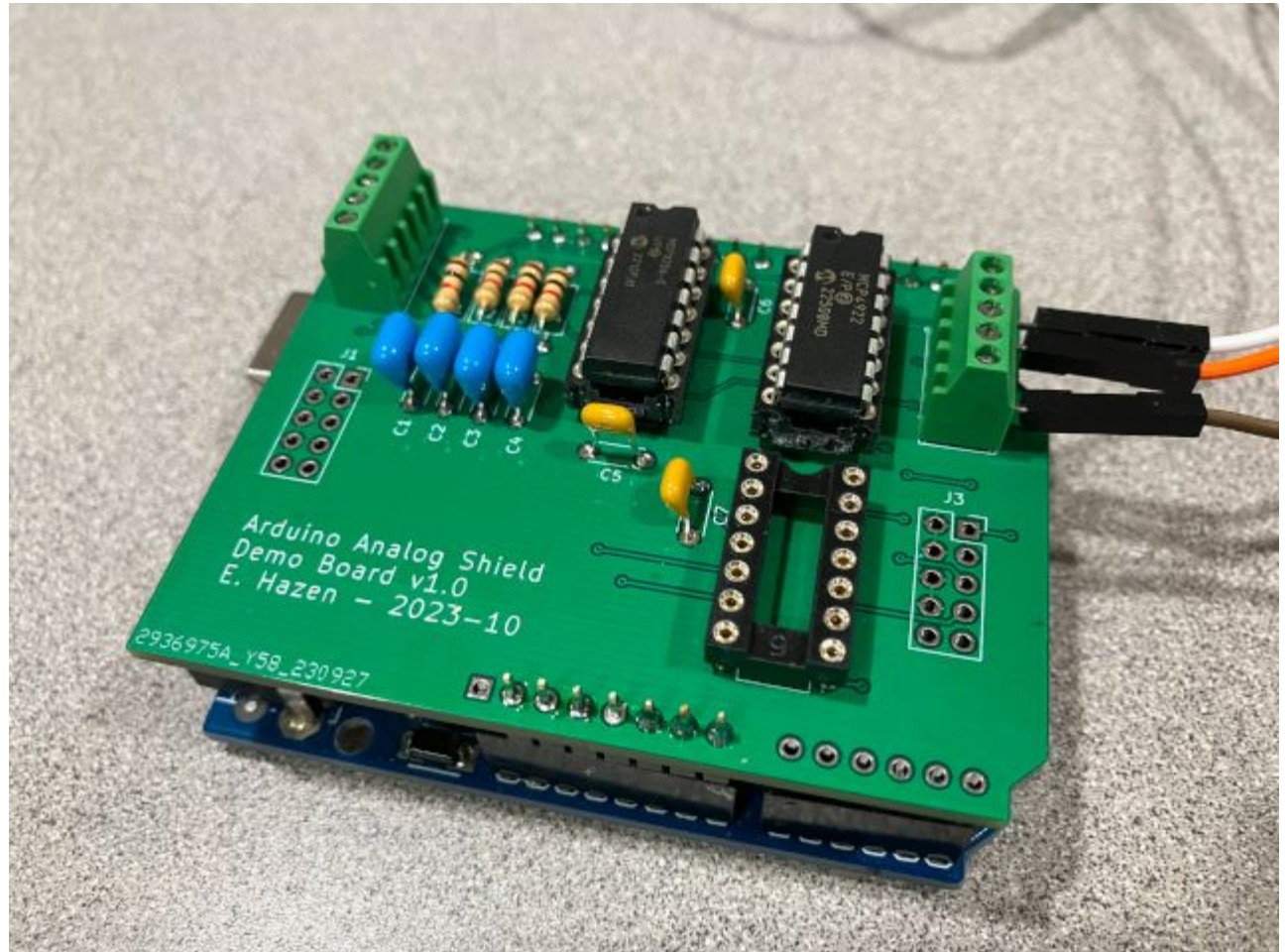Again, don't try to copy my layout, but it gives you an idea of one way the board can look.



Some hints

- KiCAD knows the layout of an Arduino Shield
Use “**File→New Project from Template**” and choose the Uno shield|
- To turn in your project:
Create a ZIP archive of the *entire project directory*
Name it like this: **Eric_Hazen_kicad_v1.zip**
Upload to the shared google drive
If you need to update it before 10/23, please upload again
With a new version number